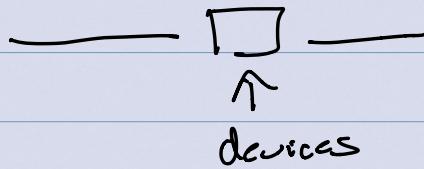


# Digital Design


## Digital Circuits - electrical

wires





### Digital Logic


wire

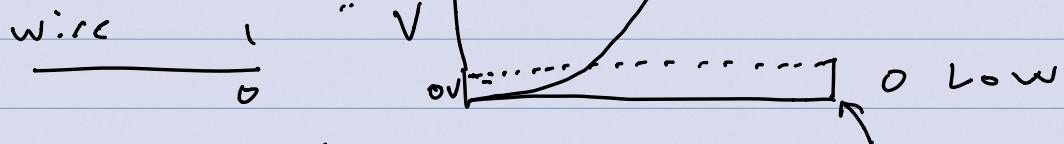

Devices  $\Rightarrow$  gates

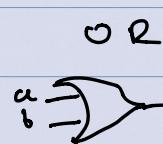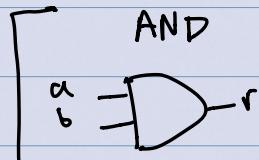

NOT

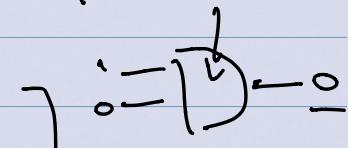

C code  $r = a \& b$

Boolean Algebra  $r = a \cdot b$

$r = \neg a$

Boolean Algebra  $[r = a \cdot b]$

$r = a + b$

$r = \bar{a}$

Logic  $r = a \wedge b$

$r = a \vee b$




$r = \neg a$

		$a \cdot b$	$r$
$a$	$b$		
0	0		0
0	1		0
1	0		0
1	1		1

		$a+b$	$r$
$a$	$b$		
0	0		0
0	1		1
1	0		1
1	1		1

$a$	$\bar{a}$	$r$
0	1	1
1	0	0

Abstraction

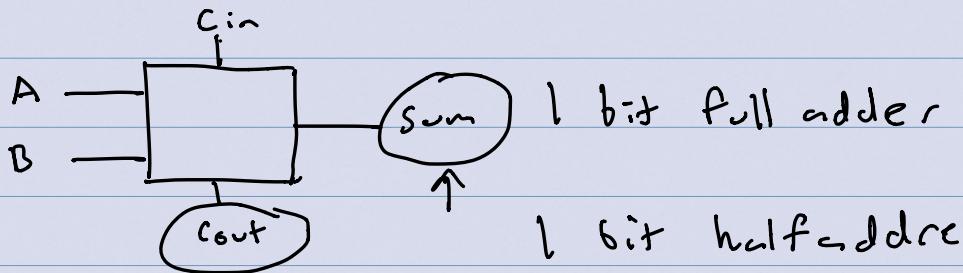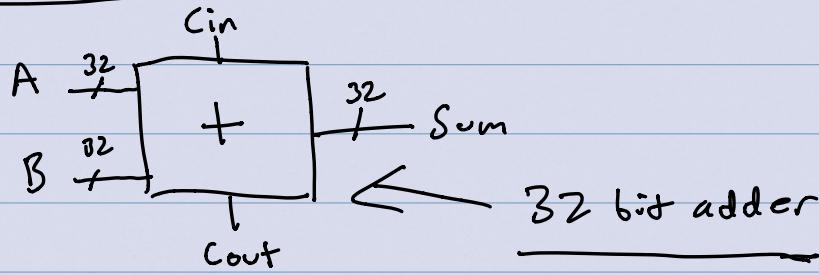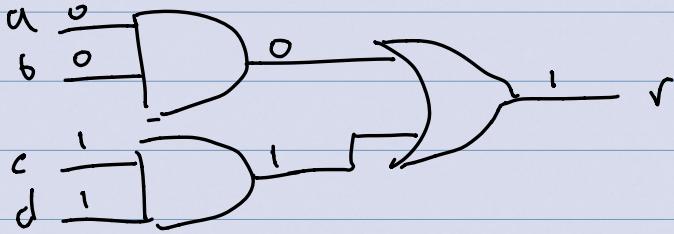

inputs

A B Cin

outputs

sum Cout



sum of products



$\xrightarrow{\text{sum plus}} \text{A} + \text{B}$  ← XOR


A B		$\text{A} + \text{B}$	
0	0	0	0
→ 0	1	1	1
→ 1	0	1	0
1	1		

③

$$\text{sum} = (\bar{A} \cdot B) + (A \cdot \bar{B})$$

A	B	$\bar{A} \cdot B$	$A \cdot \bar{B}$	$(\bar{A} \cdot B) + (A \cdot \bar{B})$
0	0	0	0	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

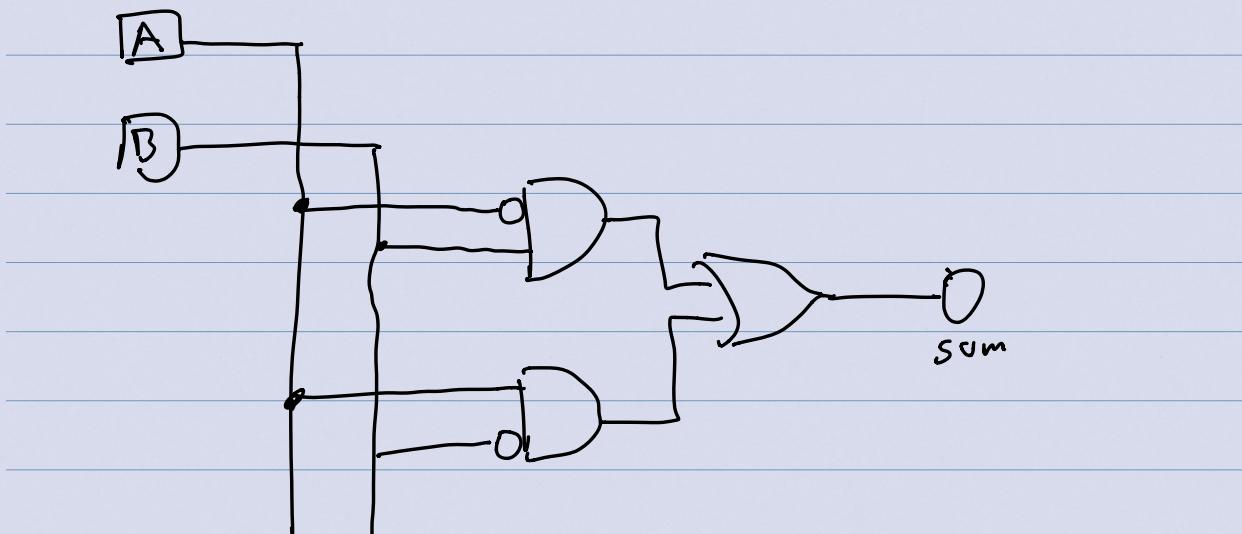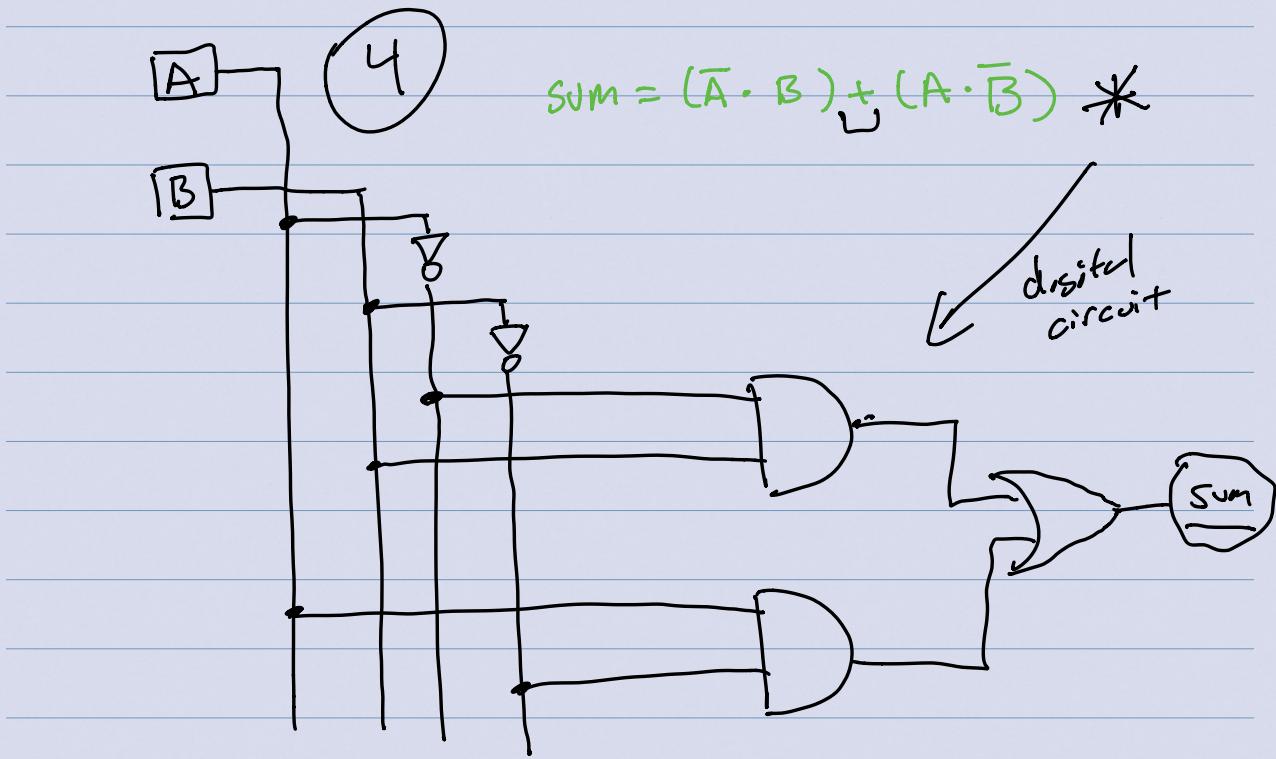

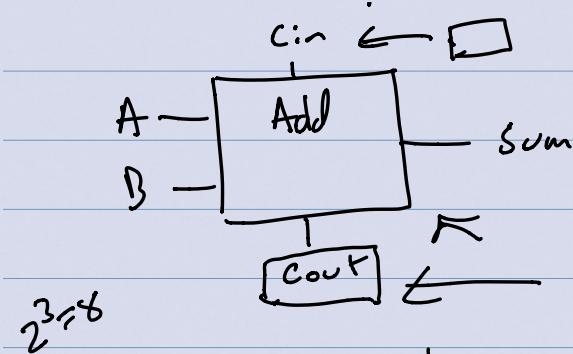


$2^3 \times 8$

$$\begin{array}{r}
 & 1 \\
 + & 1 \\
 \hline
 0
 \end{array}
 \quad
 \begin{array}{r}
 & 1 \\
 \times & 1 \\
 \hline
 0
 \end{array}$$

A	B	Cin	Sum	Cout	
0	0	0	0	0	$\frac{1}{1}$
① 0	0	1	1	0	$\frac{1}{1}$
② 1	0	0	1	0	$\frac{1}{1}$
0	1	1	0	1	
③ 1	0	0	1	0	
1	0	1	0	1	
1	1	0	0	1	
④ 1	1	1	1	1	

$$\text{Sum} = (\bar{A} \cdot \bar{B} \cdot C_{in}) + (\bar{A} \cdot B \cdot \bar{C}_{in}) + (A \cdot \bar{B} \cdot \bar{C}_{in}) + (A \cdot B \cdot C_{in})$$

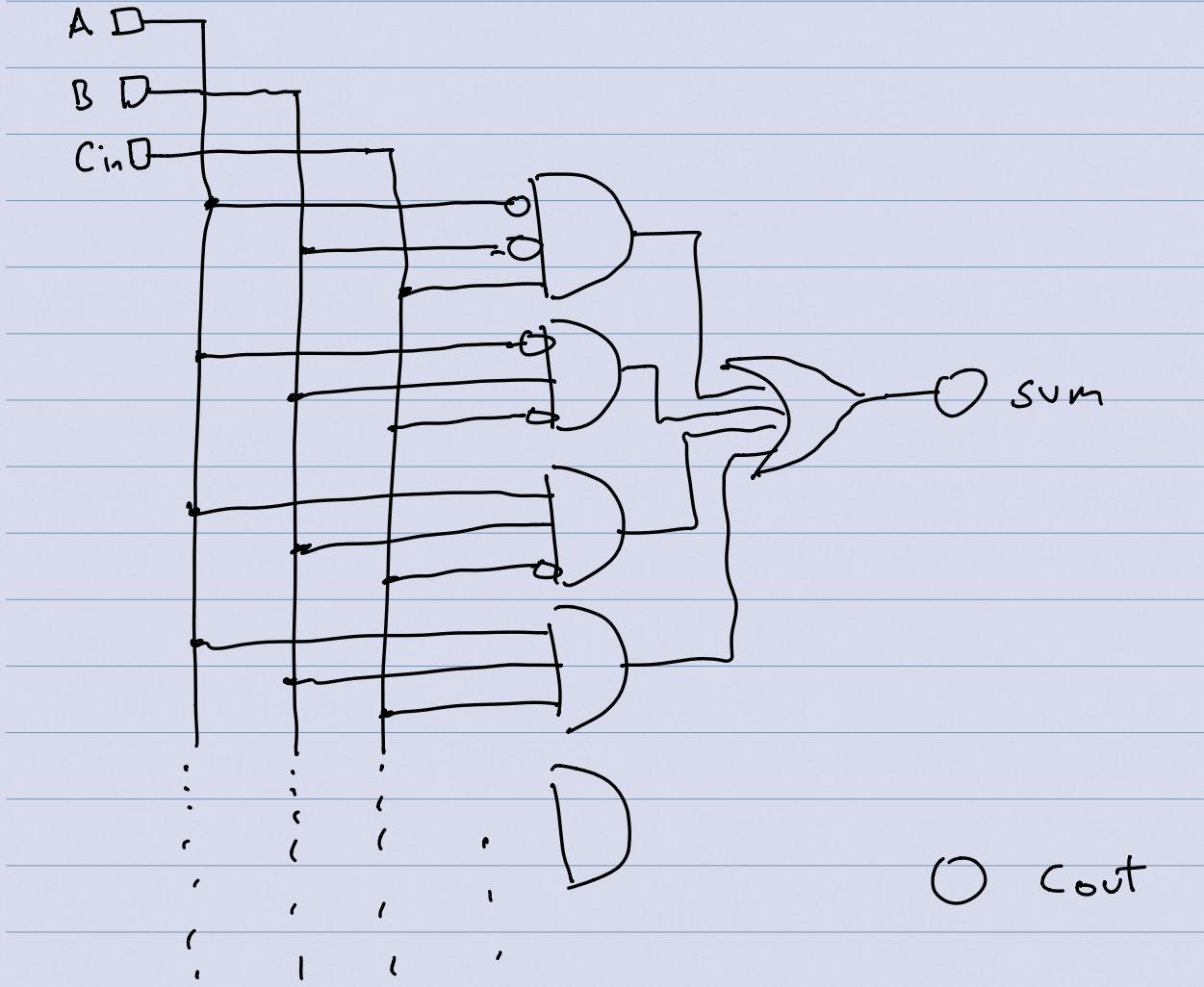

Part 3

