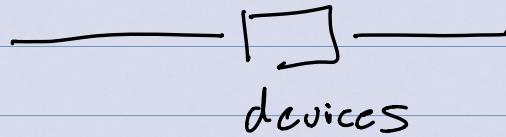


Digital Design



Digital Circuits - electrical

wires




devices

Digital Logic

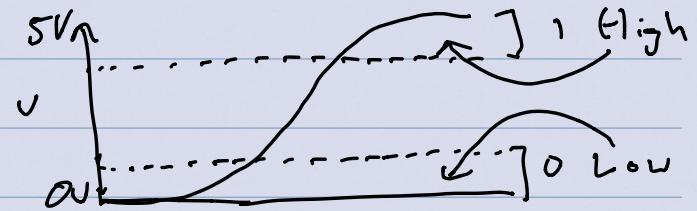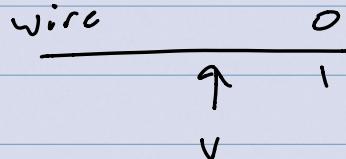

Devices \rightarrow gates

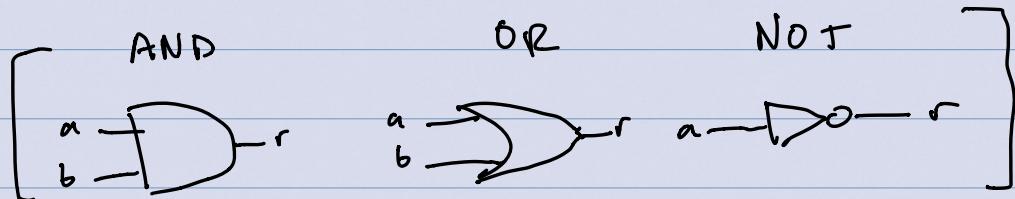

$$C \text{ code} \quad r = a \cdot b$$

$$\text{Boolean Algebra} \quad [r = a \cdot b]$$

$$\text{Logic} \quad r = a \wedge b$$

$$r = a \mid b$$

$$r = a + b$$

$$r = a \vee b$$

$$\text{NOT}$$

$$r = \sim a$$


$$r = \overline{a}$$

$$r = \neg a$$


a	b	$a \cdot b$	r
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

a	b	$a + b$	r
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	1

a	\overline{a}	r
0	1	1
1	0	0

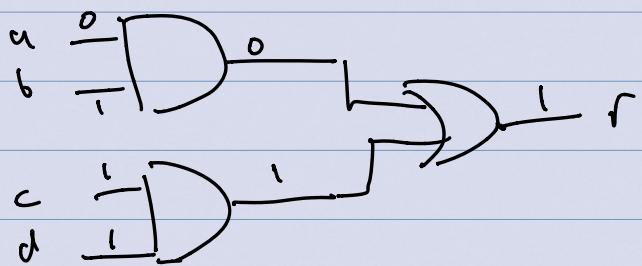


Abstraction

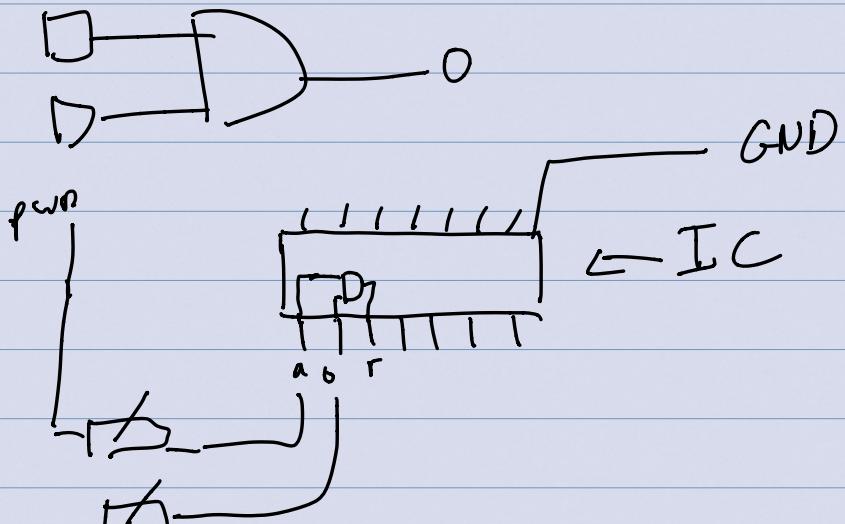


FPGA



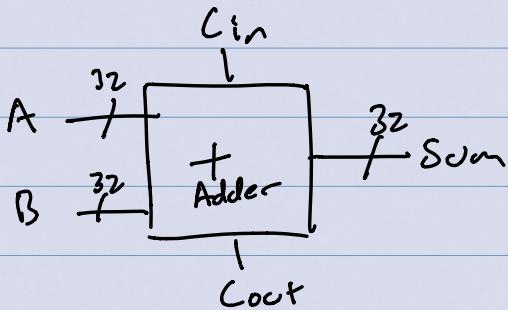

32 bit adder

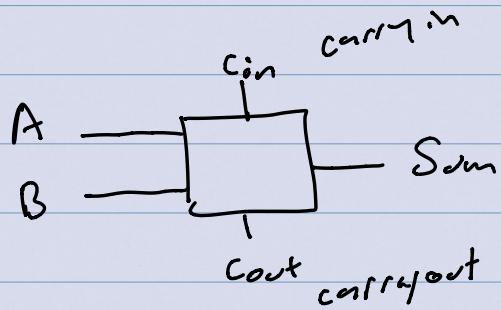

1-bit full adder


inputs

A B Cin

outputs

sum Cout

sum-of-products


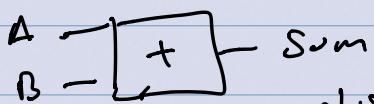



		$A + B$ Sum		XOR
		A	B	
				0
0	0	0	0	0
✓	0	1	1	1
✓	1	0	1	1
		1	1	0

$$\text{sum} = (\bar{A} \cdot B) + (A \cdot \bar{B})$$

A	B	$\bar{A} \cdot B$	$A \cdot \bar{B}$	$(\bar{A} \cdot B) + (A \cdot \bar{B})$
0	0	0	0	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0
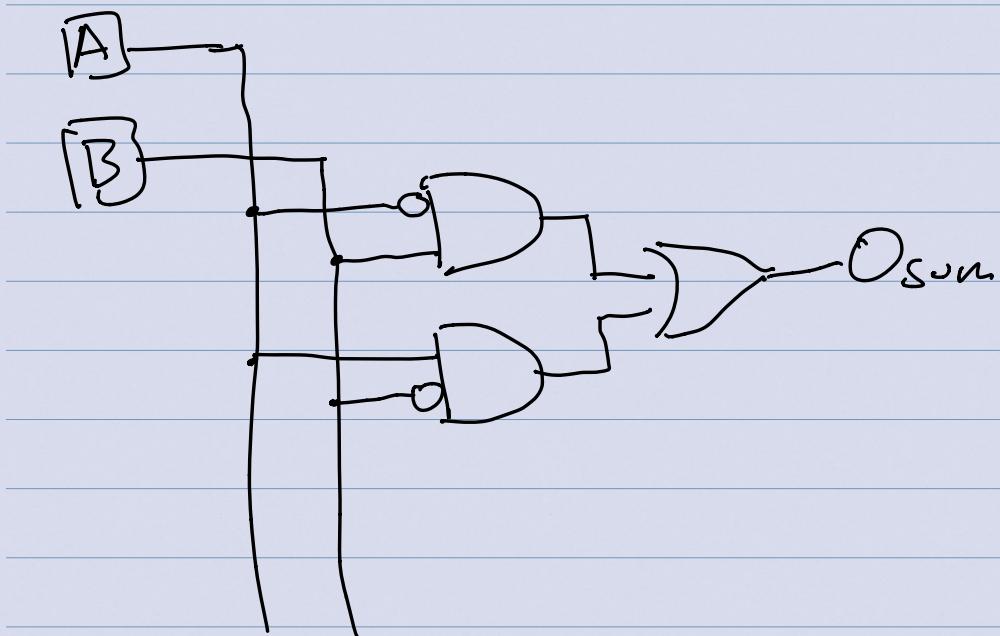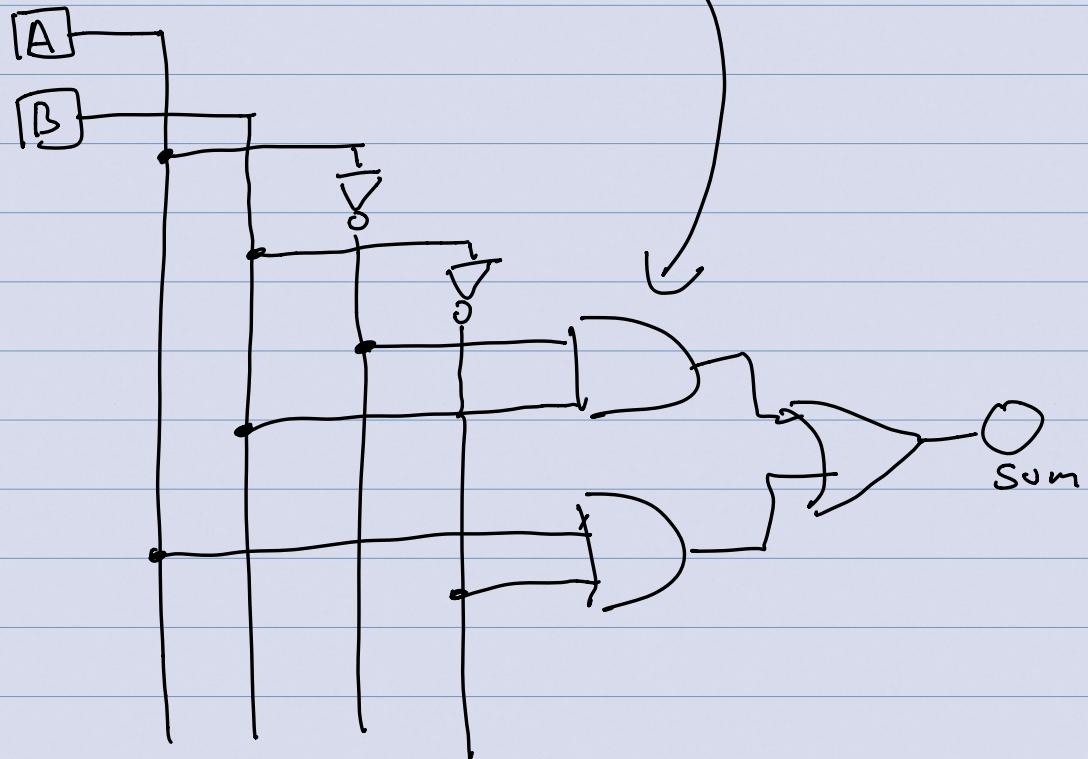
$$\text{sum} = \underline{(\bar{A} \cdot B)} + (A \cdot \bar{B})$$




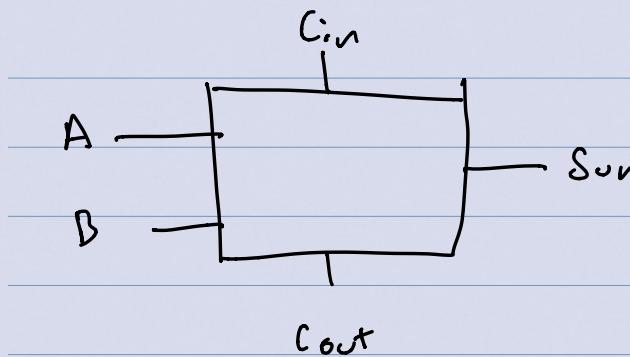

A	B	Cin	Sum	Cout	$\frac{+}{10}$
0	0	0	0	0	
✓ 0	0	1	1	0	
✓ 0	1	0	1	0	$\frac{+}{1}$
0	1	1	0	1	$\frac{+}{11}$
✓ 1	0	0	1	0	
1	0	1	0	1	
1	1	0	0	1	
✓ 1	1	1	1	1	

$$\text{sum} = (\bar{A} \cdot \bar{B} \cdot C_{in}) + (\bar{A} \cdot B \cdot \bar{C}_{in}) + (A \cdot \bar{B} \cdot \bar{C}_{in}) + (A \cdot B \cdot C_{in})$$

Part 2

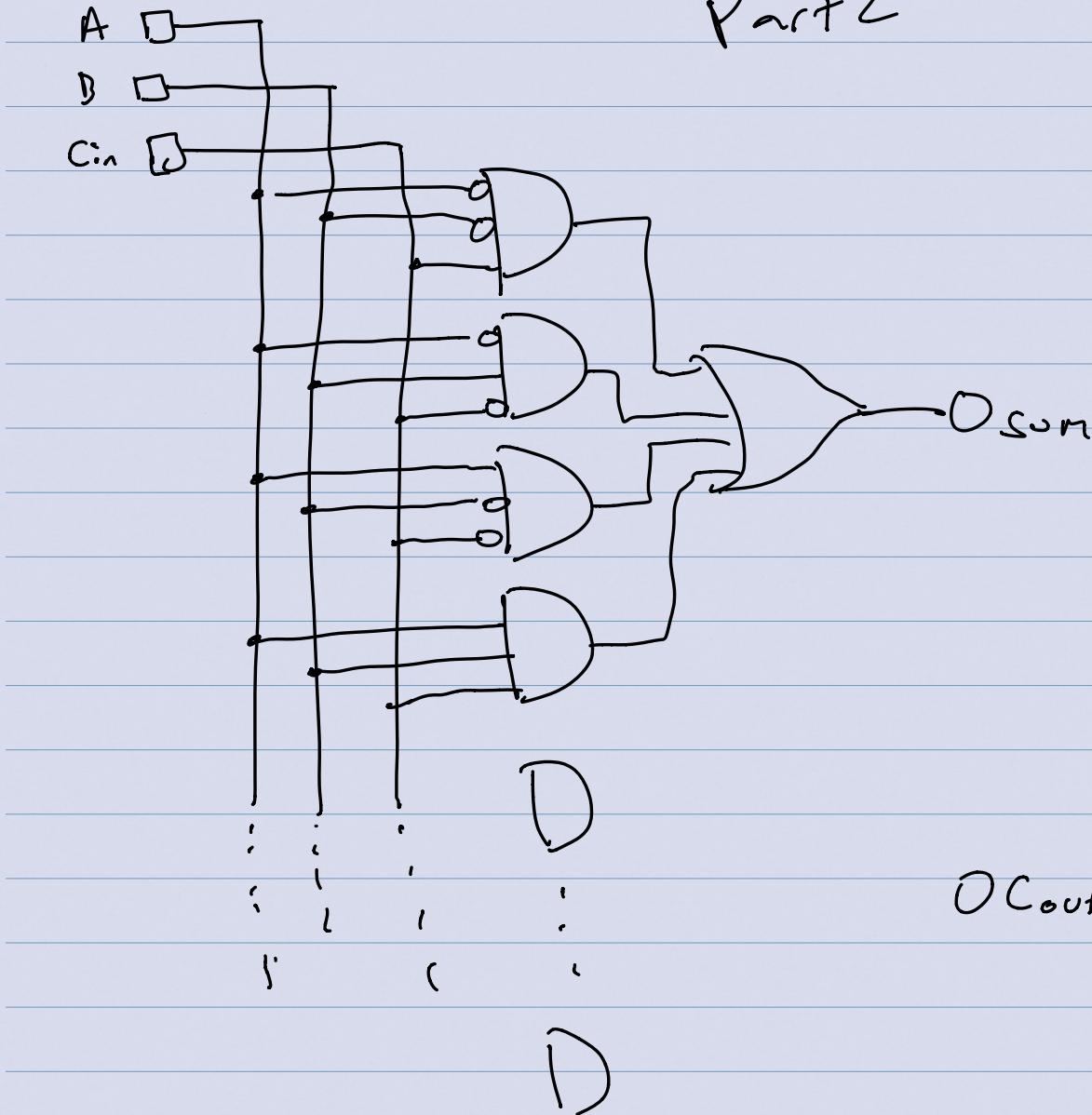

Part 3

$a \rightarrow b$, r are 2 bit values
 $0, 1, 2, 3$

$$2^4 = 16$$

$a_1 \ a_0 \ b_1 \ b_0$	$r_1 \ r_0$	Sum - & products
0 0 0 0	0 0	$r_1 =$
0 0 0 1	0 1	
0 0 1 0	1 0	$r_0 =$
0 0 1 1	1 1	
\vdots		